

LIST OF EXPERIMENT

S. NO.	EXPERIMENT NO.	AIM	PAGE NO.
1	EXPERIMENT NO. I	Synthesis & simulation of all basic logic gates using VHDL.	2
2	EXPERIMENT NO. II	Synthesis & simulation of D-flip flop using VHDL.	8
3	EXPERIMENT NO. III	Synthesis & simulation of full-adder using VHDL.	10
4	EXPERIMENT NO. IV	Synthesis & simulation of multiplexer (4:1) using VHDL.	12
5	EXPERIMENT NO. V	Synthesis & simulation of decoder (2:4) using VHDL.	14
6	EXPERIMENT NO. VI	Synthesis & simulation of 8-bit adder using VHDL.	16
7	EXPERIMENT NO. VII	Synthesis & simulation of 8-bit ALU using VHDL.	19
8	EXPERIMENT NO. VIII	Synthesis & simulation of FSM using VHDL.	28
9	EXPERIMENT NO. IX	Synthesis & simulation of 8-bit multiplier using VHDL.	32
10	EXPERIMENT NO. X	Synthesis & simulation of using 8-bit up/down counter using VHDL.	36

EXPERIMENT NO. I

AIM:-


Synthesis & simulation of all basic logic gates using VHDL.

PROGRAM:-


1) **and_gate.vhd**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity and_gate is
Port ( a : in STD_LOGIC;
      b : in STD_LOGIC;
      c : out STD_LOGIC);
end and_gate;
architecture Behavioral of and_gate is
begin
c <= a and b;
end Behavioral;
```


(a) RTL SCHEMATIC

 

 (b) SOFTWARE GENERATED INTERNAL ARCHITECTURE



(c) SIMULATION WAVEFORM

 

2) or_gate.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity or_gate is
```

```
Port ( a : in STD_LOGIC;
```

```
      b : in STD_LOGIC;
```

```
      c : out STD_LOGIC);
```

```
end or_gate;
```


```
architecture Behavioral of or_gate is
```

```
begin
```


```
c <= a or b;
```

```
end Behavioral
```


(a) RTL SCHEMATIC

 

 (b) SOFTWARE GENERATED INTERNAL ARCHITECTURE



(c) SIMULATION WAVEFORM

 

3) inverter.vhd

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity inverter is
```


NRI INSTITUTE OF INFORMATION SCIENCE & TECHNOLOGY, BHOPAL

Dept. NAME: - ELECTRONIC & TELECOMMUNICATION ENGINEERING


M.TECH LAB MANUAL

```
Port ( a : in STD_LOGIC;  
      b : out STD_LOGIC);  
  
end inverter;  
  
architecture Behavioral of inverter is  
  
begin  
  
b <= not a;  
  
end Behavioral;
```


(a) RTL SCHEMATIC

 

 (b) SOFTWARE GENERATED INTERNAL ARCHITECTURE




(c) SIMULATION WAVEFORM

 


4) xor_gate.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity xor_gate is
    Port ( a : in STD_LOGIC;
          b : in STD_LOGIC;
          c : out STD_LOGIC);
end xor_gate;
architecture Behavioral of xor_gate is
begin
    c <= a xor b;
end Behavioral;
```


(a) RTL SCHEMATIC

 

 (b) SOFTWARE GENERATED INTERNAL ARCHITECTURE



(c) SIMULATION WAVEFORM

 

EXPERIMENT NO. II

AIM:-

Synthesis & simulation of D-flip flop using VHDL.

PROGRAM:-

d_flipflop.vhd


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity d_flipflop is
    Port ( d : in STD_LOGIC;
          resetn : in STD_LOGIC;
          clock : in STD_LOGIC;
          q : out STD_LOGIC);
end d_flipflop;
architecture Behavioral of d_flipflop is
begin
    process(resetn,clock)
    begin
        if resetn='0'then
            q <= '0';
        elsif clock'event and clock ='1' then
            q <= d;
        end if;
    end process;
end Behavioral;
```

end if;


end process;

end Behavioral;


(a) RTL SCHEMATIC

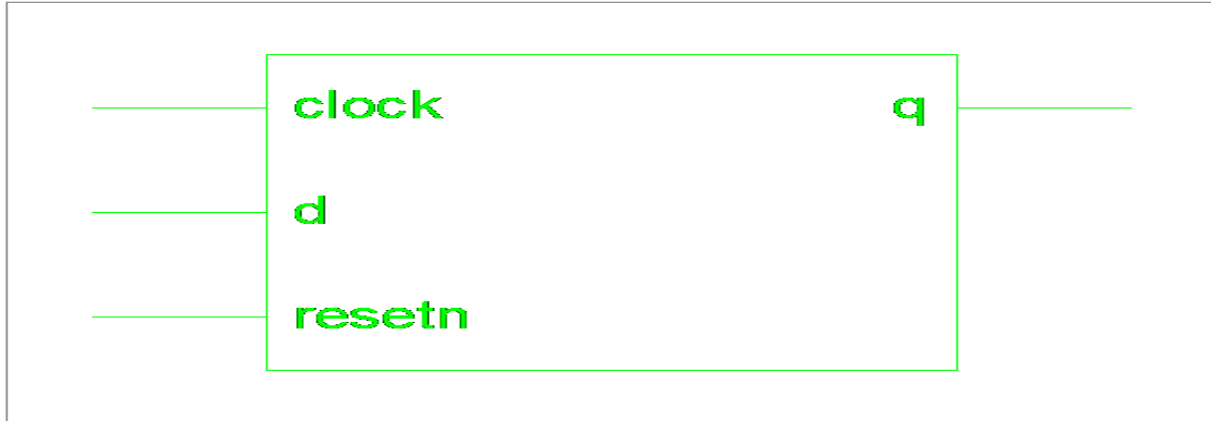

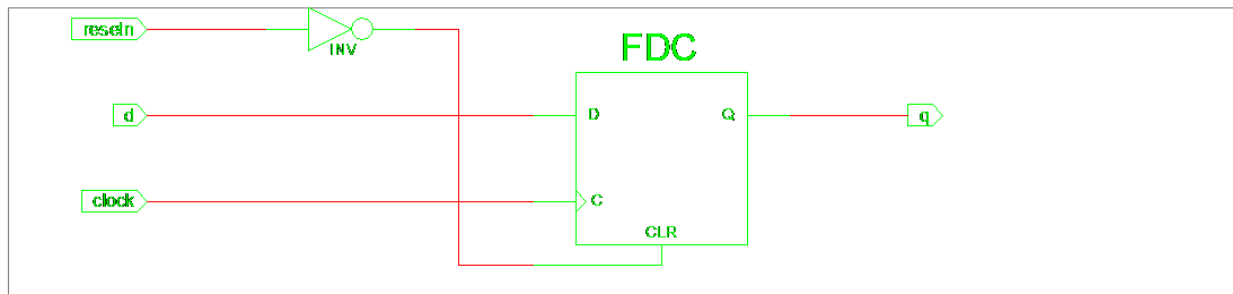(b) SOFTWARE GENERATED INTERNAL ARCHITECTURE



(c) SIMULATION WAVEFORM

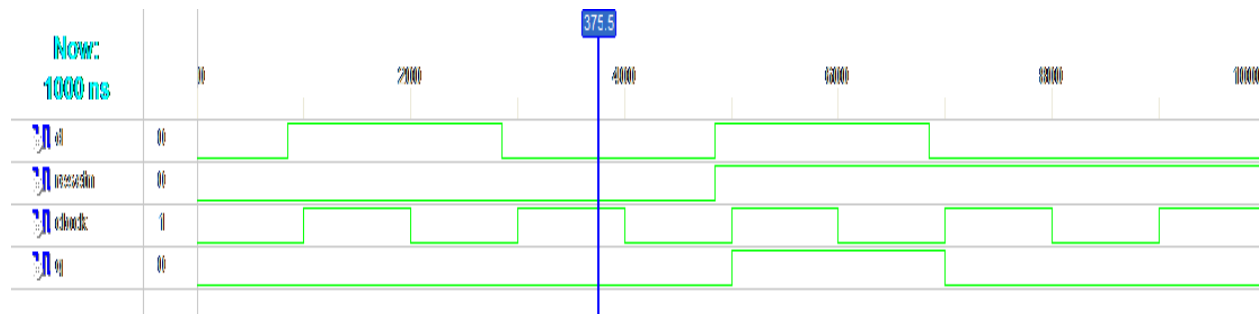

EXPERIMENT NO. III

AIM:-


Synthesis & simulation of full-adder using VHDL.

PROGRAM:-


fulladd.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity fulladd is
  Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        ci : in STD_LOGIC;
        z : out STD_LOGIC;
        co : out STD_LOGIC);
end fulladd;
architecture Behavioral of fulladd is
begin
  z <= a xor b xor ci;
  co <= (a and b) or (b and ci) or (ci and a);
end Behavioral;
```


(a) RTL SCHEMATIC

 

 (b) SOFTWARE GENERATED INTERNAL ARCHITECTURE



(c) SIMULATION WAVEFORM

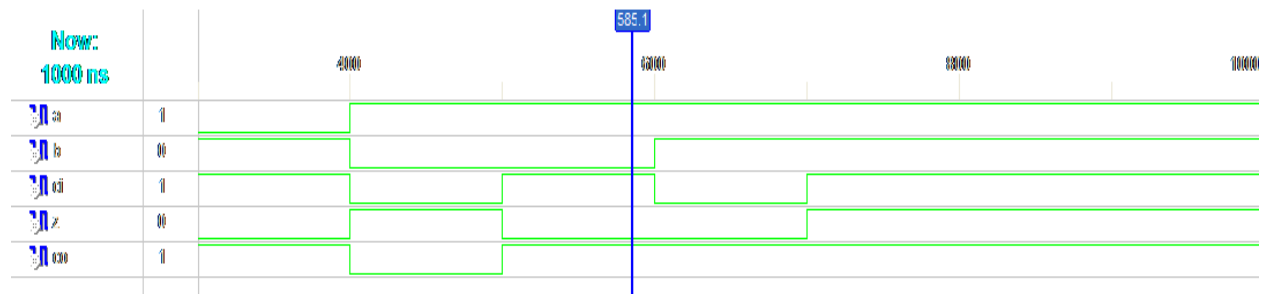

EXPERIMENT NO. IV

AIM:-

Synthesis & simulation of multiplexer (4:1) using VHDL.

PROGRAM:-

mux4to1.vhd

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity mux4to1 is

    Port ( w0 : in STD_LOGIC;

          w1 : in STD_LOGIC;

          w2 : in STD_LOGIC;

          w3 : in STD_LOGIC;

          s : in STD_LOGIC_VECTOR (1 downto 0);

          f : out STD_LOGIC);

end mux4to1;

architecture Behavioral of mux4to1 is

begin

    with s select

        f <= w0 when "00",


            w1 when "01",

            w2 when "10",
```


w3 when others;

end Behavioral;


(a) RTL SCHEMATIC

 

 (b) SOFTWARE GENERATED INTERNAL ARCHITECTURE



(c) SIMULATION WAVEFORM

 

EXPERIMENT NO. V

AIM:-

Synthesis & simulation of decoder (2:4) using VHDL.

PROGRAM:-


dec2to4.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity dec2to4 is
    Port ( w : in STD_LOGIC_VECTOR (1 downto 0);
          en : in STD_LOGIC;
          y : out STD_LOGIC_VECTOR (3 downto 0));
end dec2to4;
architecture Behavioral of dec2to4 is
    signal enw : STD_LOGIC_VECTOR (2 downto 0);
begin
    enw <= en & w;
    with enw select
        y <= "1000" when "100",
            "0100" when "101",
            "0010" when "110",
            "0001" when "111",
```


"0000" when others;

end Behavioral;


(a) RTL SCHEMATIC

 

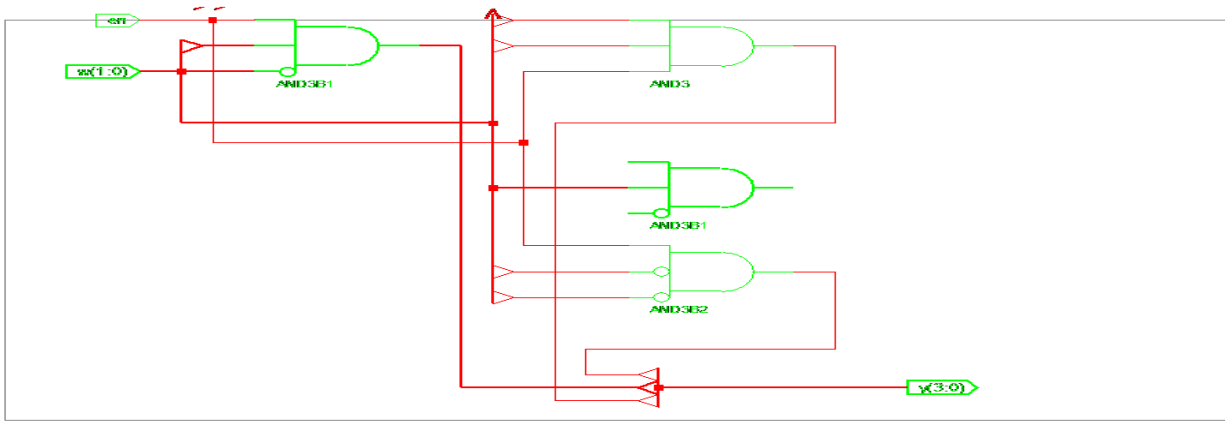(b) SOFTWARE GENERATED INTERNAL ARCHITECTURE



(c) SIMULATION WAVEFORM

 

EXPERIMENT NO. VI

AIM:-

Synthesis & simulation of 8-bit adder using VHDL.

PROGRAM:-

adder8.vhd

```
library ieee;
use ieee.std_logic_1164.all;
entity adder8 is
    generic(n:integer := 7 );
    port( A_in : in std_logic_vector(n downto 0 );
          B_in : in std_logic_vector(n downto 0 );
          SUM : out std_logic_vector(n downto 0 );
          cin : in std_logic ;
          ACY : out std_logic ;
          cout : out std_logic ) ;
end adder8 ;
architecture struct of adder8 is
    component FULLADD
    port(
        Z          : out STD_LOGIC;
        CO         : out STD_LOGIC;
        A          : in  STD_LOGIC;
        B          : in  STD_LOGIC;
        CI         : in  STD_LOGIC);
```

```
end component;

signal A_in_s :std_logic_vector(n downto 0 );
signal B_in_s :std_logic_vector(n downto 0 );
signal SUM_s :std_logic_vector(n downto 0 );
signal cin_s :std_logic_vector(n downto 0 );
signal cout_s :std_logic_vector(n downto 0 );

begin

cin_s(0) <= cin ;

    ADD0: FULLADD port map ( Z => SUM_s(0) ,
        CO => cout_s(0) ,
        A => A_in_s(0) ,
        B => B_in_s(0) ,
        CI => cin_s(0) );

G1 : for i in n downto 1 generate

    ADD1: FULLADD port map( Z => SUM_s(i) ,
        CO => cout_s(i) ,
        A => A_in_s(i) ,
        B => B_in_s(i) ,
        CI => cout_s(i-1) );

end generate ;

SUM <= SUM_S ;

cout <= cout_s(7) ;


A_in_s <= A_in ;

B_in_s <= B_in ;
```


```
ACY <= cout_s(3) ;
```

```
end struct ;
```


(a) RTL SCHEMATIC

 

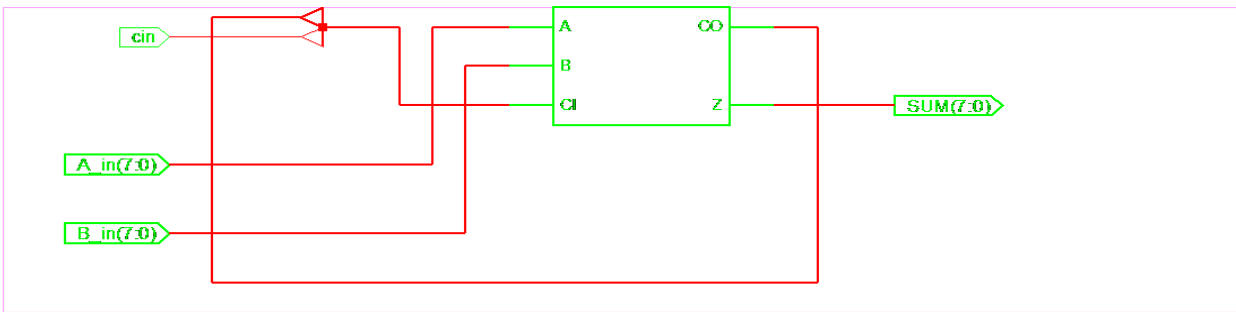(b) SOFTWARE GENERATED INTERNAL ARCHITECTURE



(c) SIMULATION WAVEFORM

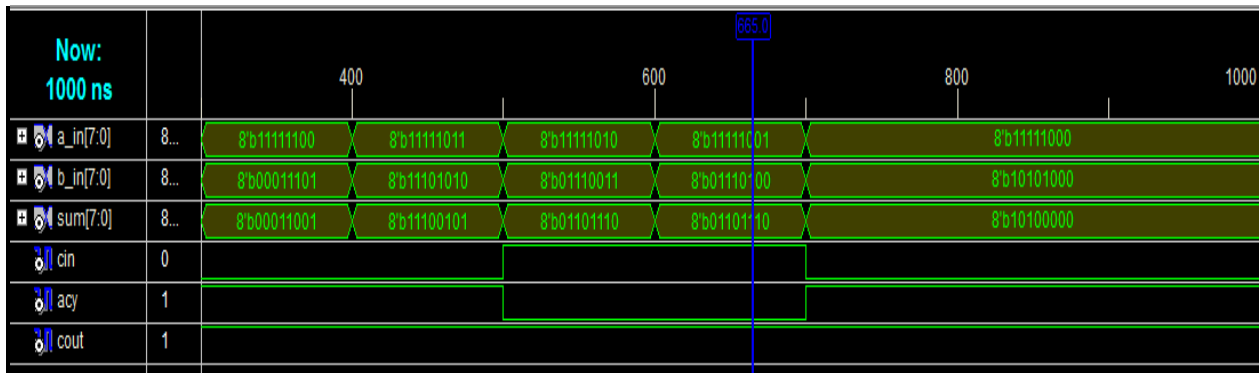

EXPERIMENT NO. VII

AIM:-

Synthesis & simulation of 8-bit ALU using VHDL.

PROGRAM:-

alu.vhd

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all ;
entity alu is
    generic ( n : integer := 7 ;
             s : integer := 3 ) ;
    port(dat_a : in std_logic_vector(n downto 0);
         dat_b : in std_logic_vector(n downto 0);
         dat_out: out std_logic_vector(n downto 0);
         cout  : out std_logic;
         ACY   : out std_logic;
         SIGN  : out std_logic;
         PARITY : out std_logic;
         ZERO  : out std_logic;
         cin   : in std_logic;
         op_sel : in std_logic_vector(s downto 0));
end alu;
```

architecture behav of alu is

```
signal nd : std_logic_vector(n downto 0);  
signal A_in_s : std_logic_vector(n downto 0);  
signal B_in_s : std_logic_vector(n downto 0);  
signal dat_b_n_s : std_logic_vector(n downto 0);  
signal dat_a_n_s : std_logic_vector(n downto 0);  
signal B_in_s_r : std_logic_vector(n downto 0);  
signal A_in_s_r : std_logic_vector(n downto 0);  
signal SUM_s : std_logic_vector(n downto 0);  
signal cout_s : std_logic ; _vector(n downto 0);
```

component ADDER8

```
port( A_in : in std_logic_vector(n downto 0);  
      B_in : in std_logic_vector(n downto 0);  
      SUM : out std_logic_vector(n downto 0);  
      cin : in std_logic ;  
      ACY : out std_logic ;  
      cout : out std_logic ) ;
```

end component;

begin

```
A_in_s <= dat_a ;  
B_in_s <= dat_b ;  
dat_b_n_s <= not(dat_b) ;  
dat_a_n_s <= not(dat_a) ;  
A8_1 : adder8 port map (A_in => A_in_s_r ,
```

NRI INSTITUTE OF INFORMATION SCIENCE & TECHNOLOGY, BHOPAL

Dept. NAME: - ELECTRONIC & TELECOMMUNICATION ENGINEERING

M.TECH LAB MANUAL

```
B_in => B_in_s_r ,
SUM => SUM_s ,
cin => cin ,
ACY => ACY ,
cout => cout_s) ;

process(dat_a,dat_b,op_sel,A_in_s,B_in_s,dat_b_n_s,SUM_s)
variable dat_xor_res:std_logic_vector(n downto 0) ;
variable dat_shr_res:std_logic_vector(n downto 0) ;
variable dat_xnor_res:std_logic_vector(n downto 0);
variable dat_and_res:std_logic_vector(n downto 0);
variable dat_nand_res:std_logic_vector(n downto 0);
variable dat_or_res:std_logic_vector(n downto 0);
variable dat_nor_res:std_logic_vector(n downto 0);
variable dat_out_var:std_logic_vector(n downto 0);
variable op_sel_int : integer := 0 ;

begin

op_sel_int := CONV_INTEGER(op_sel);

for i in n downto 0 loop

dat_xor_res(i) := dat_a(i) xor dat_b(i);

end loop;

for i in n-1 downto 0 loop

dat_shr_res(i) := dat_a(i+1) ;

end loop;
```

```
dat_shr_res(7) := '0' ;  
for i in n downto 0 loop  
    dat_xnor_res(i) := not (dat_a(i) xor dat_b(i));  
end loop;  
for i in n downto 0 loop  
    dat_and_res(i) := dat_a(i) and dat_b(i);  
end loop;  
for i in n downto 0 loop  
    dat_nand_res(i) := not (dat_a(i) and dat_b(i));  
end loop;  
for i in n downto 0 loop  
    dat_or_res(i) := dat_a(i) or dat_b(i);  
end loop;  
for i in n downto 0 loop  
    dat_nor_res(i) := not (dat_a(i) or dat_b(i));  
end loop;  
case op_sel_int is  
    when 1 =>  
        dat_out_var := dat_xor_res ;  
        B_in_s_r <= B_in_s ;  
        A_in_s_r <= A_in_s ;  
        cout <= '0' ;  
    when 2 =>  
        dat_out_var := dat_xnor_res ;
```

```
B_in_s_r <= B_in_s ;  
A_in_s_r <= A_in_s ;  
cout <= '0' ;  
when 3 =>  
    dat_out_var := dat_and_res ;  
    B_in_s_r <= B_in_s ;  
    A_in_s_r <= A_in_s ;  
    cout <= '0' ;  
when 4 =>  
    dat_out_var := dat_nand_res ;  
    B_in_s_r <= B_in_s ;  
    A_in_s_r <= A_in_s ;  
    cout <= cout_s ;  
when 5 =>  
    dat_out_var := dat_or_res ;  
    B_in_s_r <= B_in_s ;  
    A_in_s_r <= A_in_s ;  
    cout <= '0' ;  
when 6 =>  
    dat_out_var := dat_nor_res ;  
    B_in_s_r <= B_in_s ;  
    A_in_s_r <= A_in_s ;  
    cout <= '0' ;
```

```
when 0 => -- add A + B
```

```
B_in_s_r <= B_in_s ;
```

```
dat_out_var := SUM_s ;
```

```
A_in_s_r <= A_in_s ;
```

```
cout <= cout_s ;
```

```
when 7 => -- sub A - B
```

```
B_in_s_r <= dat_b_n_s ;
```

```
dat_out_var := SUM_s ;
```

```
A_in_s_r <= A_in_s ;
```

```
cout <= cout_s ;
```

```
when 8 => -- not not(A)
```

```
B_in_s_r <= "00000000" ;
```

```
dat_out_var := SUM_s ;
```

```
A_in_s_r <= dat_a_n_s ;
```

```
cout <= cout_s ;
```

```
when 9 => -- inr REG + 1
```

```
B_in_s_r <= B_in_s ;
```

```
dat_out_var := SUM_s ;
```

```
A_in_s_r <= "00000000" ;
```

```
cout <= cout_s ;
```

```
when 10 => -- dcr REG - 1
```

```
B_in_s_r <= "11111110" ;
```

```
dat_out_var := SUM_s ;
```

```
A_in_s_r <= B_in_s ;
```

```
cout <= cout_s ;  
when 11 => -- shl A <- shl(A)  
B_in_s_r <= A_in_s ;  
dat_out_var := SUM_s ;  
A_in_s_r <= A_in_s ;  
cout <= cout_s ;  
when 12 => -- zero/clear  
B_in_s_r <= "00000000" ;  
dat_out_var := SUM_s ;  
A_in_s_r <= "00000000";  
cout <= cout_s ;  
when 13 =>  
dat_out_var := dat_shr_res ; -- SHR(A)  
B_in_s_r <= B_in_s ;  
A_in_s_r <= A_in_s ;  
cout <= cout_s ;  
when others =>  
dat_out_var := SUM_s ;  
B_in_s_r <= "00000000" ;  
A_in_s_r <= "00000000";  
cout <= cout_s ;  
end case ;  
dat_out <= dat_out_var ;
```

NRI INSTITUTE OF INFORMATION SCIENCE & TECHNOLOGY, BHOPAL

Dept. NAME: - ELECTRONIC & TELECOMMUNICATION ENGINEERING

M.TECH LAB MANUAL

```
PARITY <= dat_out_var(0) xor dat_out_var(1) xor dat_out_var(2) xor dat_out_var(3) xor  
dat_out_var(4) xor dat_out_var(5) xor dat_out_var(6) xor dat_out_var(7) ;
```

```
nd <= dat_out_var ;
```


```
end process;
```

```
ZERO <= not (nd(0) and nd(1) and nd(2) and nd(3) and nd(4) and nd(5) and nd(6) and nd(7)) ;
```


```
SIGN <= nd(7) ;
```

```
end behav;
```


(a) RTL SCHEMATIC

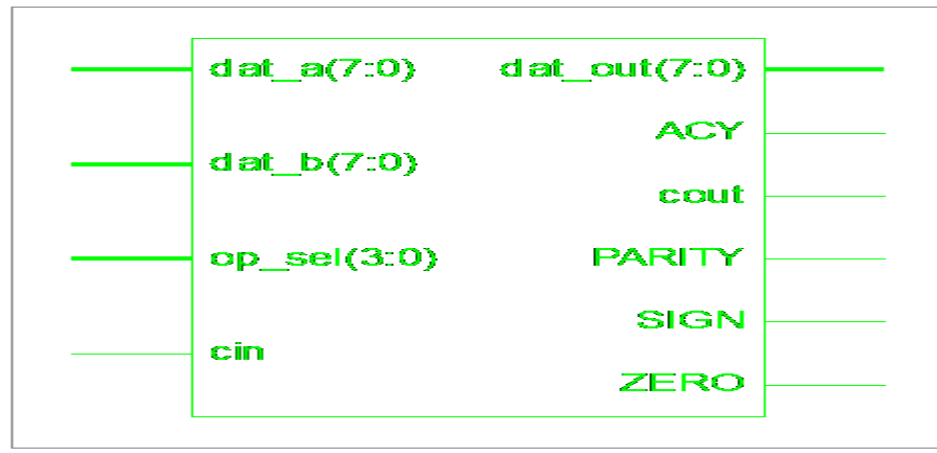

 (b) SOFTWARE GENERATED INTERNAL ARCHITECTURE



(c) SIMULATION WAVEFORM

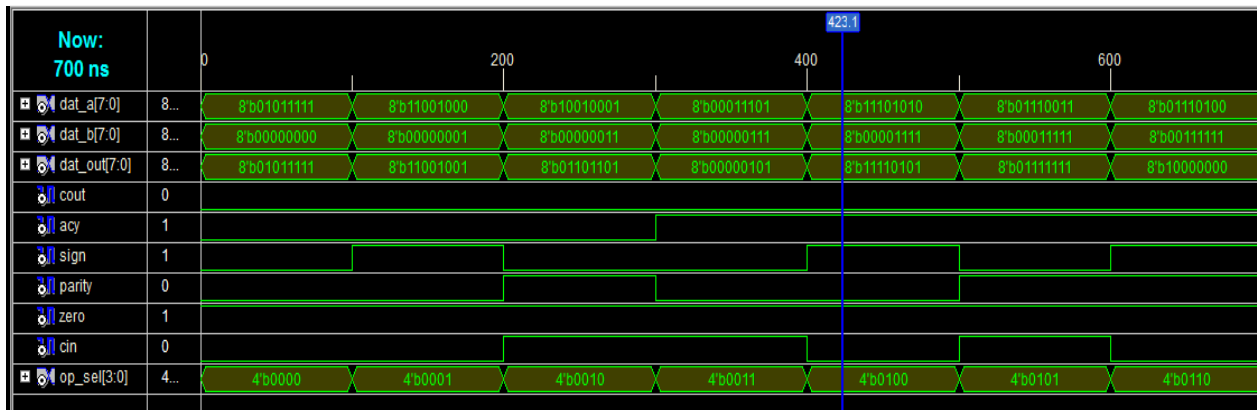

EXPERIMENT NO. VIII

AIM:-

Synthesis & simulation of FSM using VHDL.

PROGRAM:-

FSM.vhd

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity FSM is
    Port ( clk : in STD_LOGIC;
          reset : in STD_LOGIC;
          a : in STD_LOGIC;
          x : out STD_LOGIC;
          y : out STD_LOGIC);
end FSM;
architecture Behavioral of FSM is
    type statetype is (S0, S1, S2, S3, S4);
    signal state, nextstate: statetype;
begin
    -- state register
    process (clk, reset) begin
        if reset = '1' then state <= S0;
        elsif clk'event and clk = '1' then state <= nextstate;
```

```
end if;

end process;

-- next state logic

process (state, a) begin
case state is
when S0 => if a = '1' then nextstate <= S3;
           else nextstate <= S1;
           end if;
when S1 => if a = '1' then nextstate <= S3;
           else nextstate <= S2;
           end if;
when S2 => if a = '1' then nextstate <= S3;
           else nextstate <= S2;
           end if;
when S3 => if a = '1' then nextstate <= S4;
           else nextstate <= S1;
           end if;
when S4 => if a = '1' then nextstate <= S4;
           else nextstate <= S1;
           end if;
when others => nextstate <= S0;
end case;
end process;

--output logic
```

$x \leq '1'$ when ((state = S1 or state = S2) and a = '1') or


((state = S3 or state = S4) and a = '1')

else '1';


$y \leq '1'$ when (state = S2 and a = '1') or (state = S4 and a='1')

else '1';


end Behavioral;

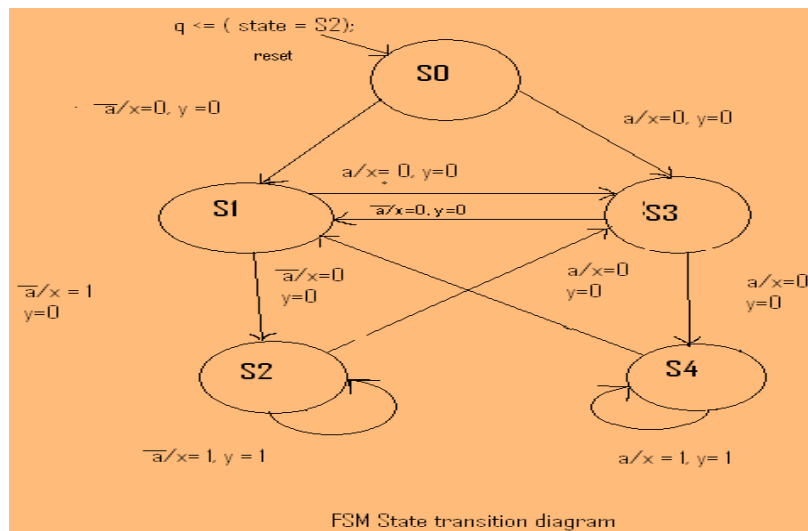


(a) RTL SCHEMATIC

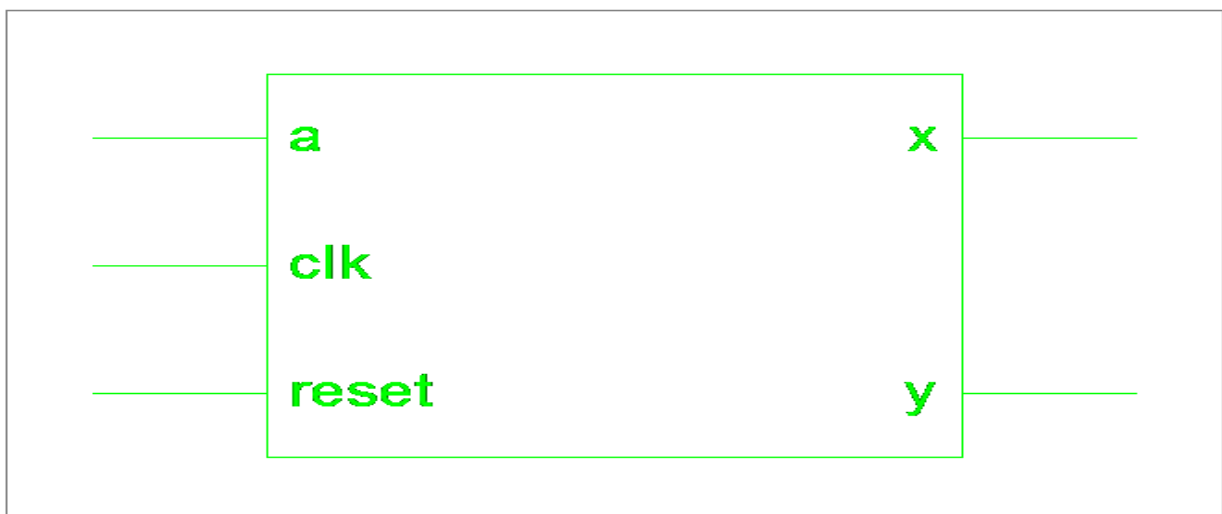

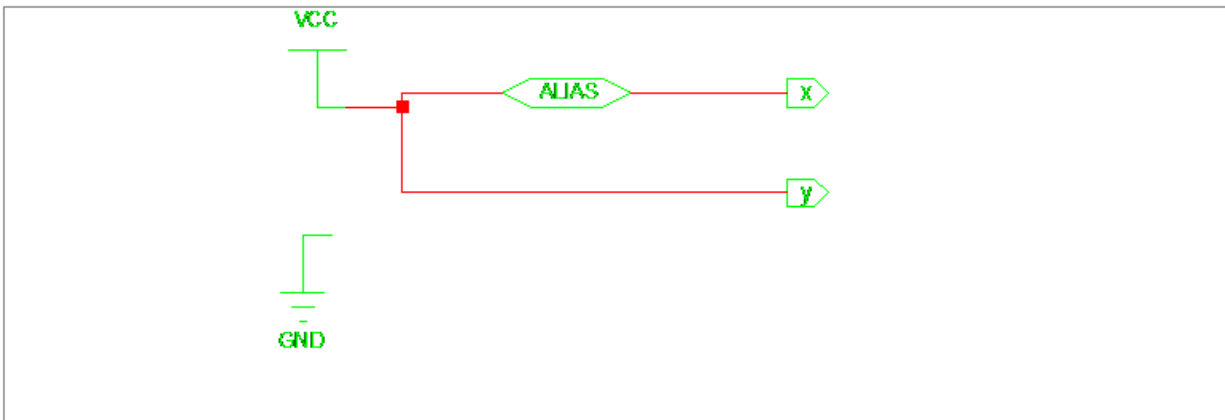(b) SOFTWARE GENERATED INTERNAL ARCHITECTURE



(c) SIMULATION WAVEFORM

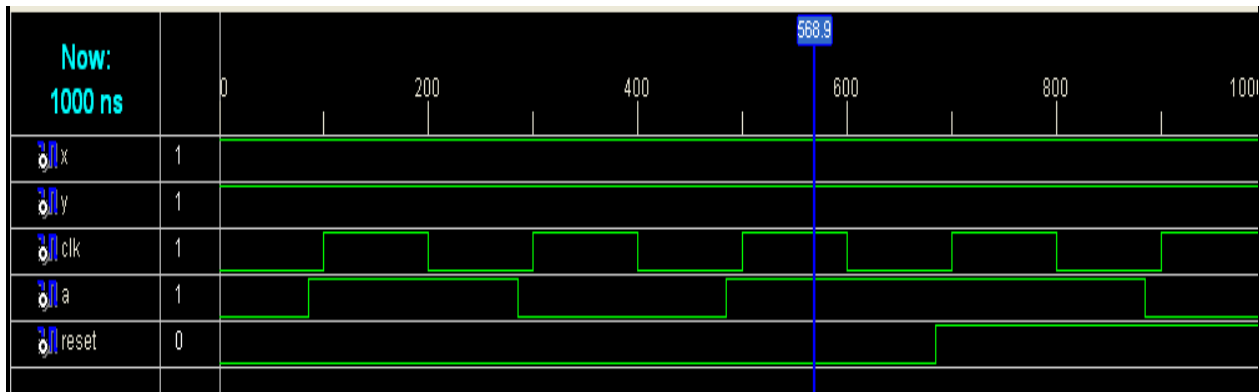

EXPERIMENT NO. IX

AIM:-

Synthesis & simulation of 8- bit multiplier using VHDL.

PROGRAM:-

MULTIPLIER 8.VHD

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity multiplier_8 is

    Port ( clk : in STD_LOGIC;

          a : in STD_LOGIC_VECTOR (7 downto 0);

          b : in STD_LOGIC_VECTOR (7 downto 0);

          y : out STD_LOGIC_VECTOR (15 downto 0));

end multiplier_8;

architecture Behavioral of multiplier_8 is

begin

p1: process(clk)

variable n0,n1,n2,n3,n4,n5,n6,n7: std_logic_vector(15 downto 0);

variable m: std_logic_vector(7 downto 0);

begin

m:="00000000";


if clk'event and clk='1' then

if a(0)<='0' then
```


```
n0:="0000000000000000";  
else  
n0:=m&b;  
end if;  
if a(1)<='0' then  
n1:="0000000000000000";  
else  
n1:=m(7 downto 1)&b&m(0);  
end if;  
if a(2)<='0' then  
n2:="0000000000000000";  
else  
n2:=m(7 downto 2)&b&m(1 downto 0);  
end if;  
if a(3)<='0' then  
n3:="0000000000000000";  
else  
n3:=m(7 downto 3)&b&m(2 downto 0);  
end if;  
if a(4)<='0' then  
n4:="0000000000000000";  
else  
n4:=m(7 downto 4)&b&m(3 downto 0);  
end if;  
if a(5)<='0' then
```

```
n5:="0000000000000000";  
else  
n5:=m(7 downto 5)&b&m(4 downto 0);  
end if;  
if a(6)<='0' then  
n6:="0000000000000000";  
else  
n6:=m(7 downto 6)&b&m(5 downto 0);  
end if;  
if a(7)<='0' then  
n7:="0000000000000000";  
else  
n7:=m(7)&b&m(6 downto 0);  
end if;  
y<=n0+n1+n2+n3+n4+n5+n6+n7;  
end if;  
end process p1;  
end Behavioral;
```


(a) RTL SCHEMATIC

 

 (b) SOFTWARE GENERATED INTERNAL ARCHITECTURE



(c) SIMULATION WAVEFORM

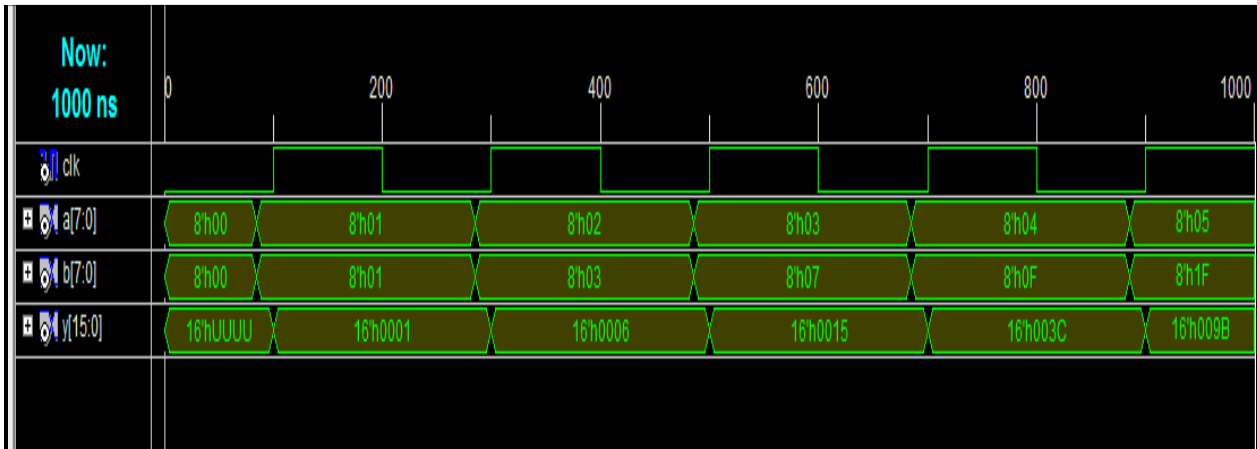

EXPERIMENT NO. X

AIM:-

Synthesis & simulation of using 8-bit up/down counter using VHDL.

PROGRAM:-

BIT8CNT.VHD

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity BIT8CNT is

Port (EN : in STD_LOGIC;

CLR : in STD_LOGIC;

CLK : in STD_LOGIC;

CE : in std_logic;

Carry : out std_logic;

COUNTER : out STD_LOGIC_VECTOR (7 downto 0);

UD : in std_logic);

end BIT8CNT;

architecture Behavioral of BIT8CNT is

component BIT4CNT

PORT (EN : in STD_LOGIC;

CLK : in STD_LOGIC;

CLR : in STD_LOGIC;

NRI INSTITUTE OF INFORMATION SCIENCE & TECHNOLOGY, BHOPAL

Dept. NAME: - ELECTRONIC & TELECOMMUNICATION ENGINEERING

M.TECH LAB MANUAL

CE : in std_logic;

CARRY: out std_logic;

CNT : out std_logic_vector(3 downto 0);

UD : in std_logic);

end component;

signal C0_IN,C0_OUT : std_logic;

begin

u0: BIT4CNT Port map(
CLK=>CLK,CLR=>CLR,CE=>CE,EN=>EN,CARRY=>C0_OUT,CNT=>COUNTER(
3 downto 0),UD=>UD);

u1: BIT4CNT Port map(
CLK=>CLK,CLR=>CLR,CE=>CE,EN=>C0_IN,CARRY=>Carry,CNT=>COUNTER(
7 downto 4),UD=>UD);

C0_IN <= C0_OUT AND EN;

end Behavioral;

BIT4CNT.VHD

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity BIT4CNT is

Port (EN : in STD_LOGIC;

CLK : in STD_LOGIC;

CLR : in STD_LOGIC;

NRI INSTITUTE OF INFORMATION SCIENCE & TECHNOLOGY, BHOPAL

Dept. NAME: - ELECTRONIC & TELECOMMUNICATION ENGINEERING

M.TECH LAB MANUAL

CE : in std_logic;

CARRY: out std_logic;

CNT : out std_logic_vector(3 downto 0);

UD : in std_logic);

end BIT4CNT;

architecture Behavioral of BIT4CNT is

component EX3

Port(T: in std_logic;

CLR : in std_logic;

CLK : in std_logic;

CE : in std_logic;

Q: out std_logic);

end component;

signal c0,c1,c2: std_logic;

signal Q :std_logic_vector(3 downto 0);

begin

u0 : EX3 Port map (CLK=>CLK,CLR=>CLR,CE =>CE,T=>EN,Q=>Q(0));

u1 : EX3 Port map (CLK=>CLK,CLR=>CLR,CE =>CE,T=>c0,Q=>Q(1));

u2 : EX3 Port map (CLK=>CLK,CLR=>CLR,CE =>CE,T=>c1,Q=>Q(2));

u3 : EX3 Port map (CLK=>CLK,CLR=>CLR,CE =>CE,T=>c2,Q=>Q(3));

process(EN,CLK,CE,UD,Q,c0,c1,c2)

begin

if(UD = '1') then

c0<=EN and Q(0);

NRI INSTITUTE OF INFORMATION SCIENCE & TECHNOLOGY, BHOPAL

Dept. NAME: - ELECTRONIC & TELECOMMUNICATION ENGINEERING

M.TECH LAB MANUAL

```
c1<=c0 and Q(1);
c2<=c1 and Q(2);
CARRY<=c2 and Q(3);
else
c0<=EN and not Q(0);
c1<=c0 and not Q(1);
c2<=c1 and not Q(2);
CARRY<=c2 and not Q(3);
end if;
CNT <= Q;
end process;
end Behavioral;
```

EX3.VHD

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity EX3 is
Port ( T : in STD_LOGIC;
CLR : in STD_LOGIC;
CLK : in STD_LOGIC;
CE : in std_logic;
Q : out STD_LOGIC);
```

```
end EX3;

architecture Behavioral of EX3 is

begin

    process(CLK,CLR)

        variable temp : std_logic := '0';

        begin

            if(CLR = '1') then

                temp := '0';

            elsif(CLK'EVENT and CLK = '1') then

                if(CE = '1') then

                    if(T = '0') then

                        temp := temp;

                    else

                        temp := not temp;

                    end if;

                end if;


            end if;

            Q <= temp;


        end process;

    end Behavioral;
```

(a) RTL SCHEMATIC

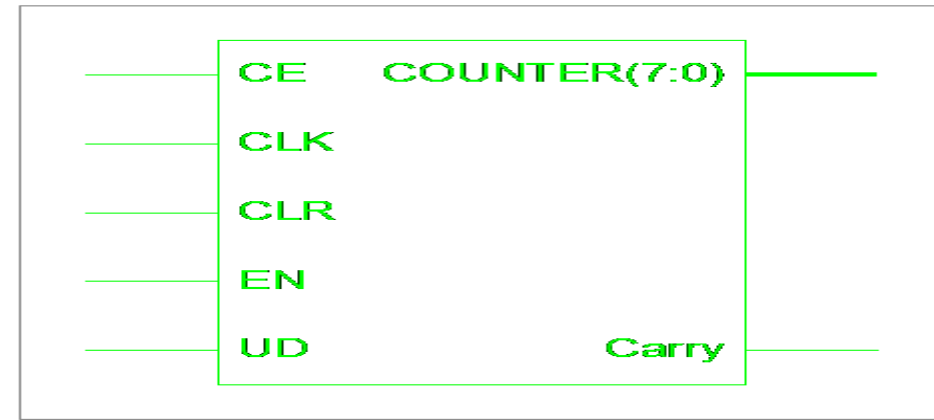

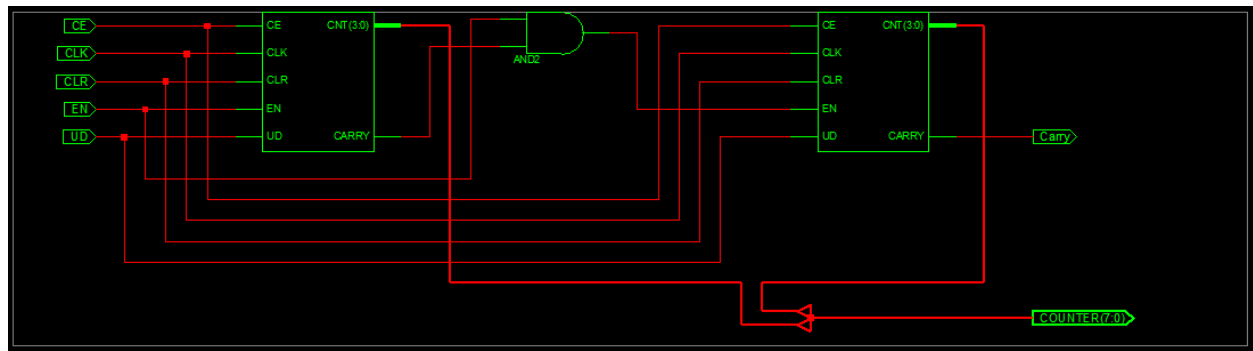(b) SOFTWARE GENERATED INTERNAL ARCHITECTURE



(c) SIMULATION WAVEFORM

